

# Quantization of electrical circuits


(1)

Goal: given an electrical circuit composed of inductors and capacitors, find the system Hamiltonian.

N.B Here no Josephson Junction (for  $ndv$ ) and no resistors.

Lumped element representation:

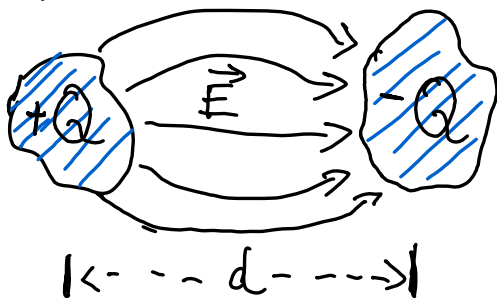- consider two metallic islands charged with  $\pm Q$



$\vec{E}$  electric field

$d$  characteristic length of the circuit

In a static configuration charges arrange on the surface of the conductor and the electric field vanishes inside the metal.

The time to reach a static charge configuration ( $\tau \sim d/c$ ), with  $c$  the velocity of the light.


If  $Q(t)$  changes slowly compared to  $\tau$ , the electric field follows quasi-instantaneously.

The energy required to move one unit charge from one to the other island is path-independent and given by the voltage  $V$ .  $V = Q/C$   $C$  is the capacitance; it depends on geometry and dielectric medium.

$\Rightarrow$  Total energy stored in the electric field

$$E_{el} = \int_0^Q dQ' V(Q') = \int_0^Q dQ' \frac{Q'}{C} = \frac{Q^2}{2C}$$

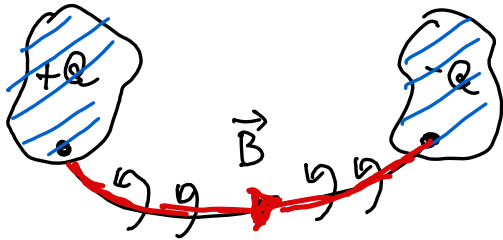• Now let's consider an additional wire connecting the 2 islands



$$I = -\dot{Q}$$

$\Phi_B = L I \rightarrow$  current  
 $\downarrow$   
 Inductance (geometry-dependent)  
 magnetic flux

Energy stored in magnetic field  $\vec{B}$ :



$$E_{mag} = \int_0^I dI' \Phi(I') = \frac{1}{2} L I^2 = \frac{\Phi^2}{2L}$$

$$\Phi_B(t) = \int_0^t V(t') dt'$$

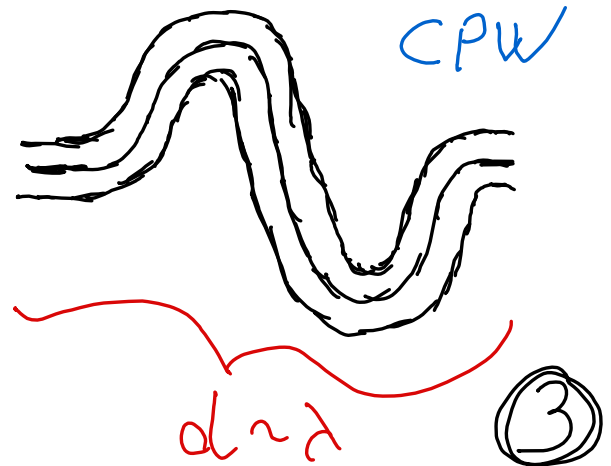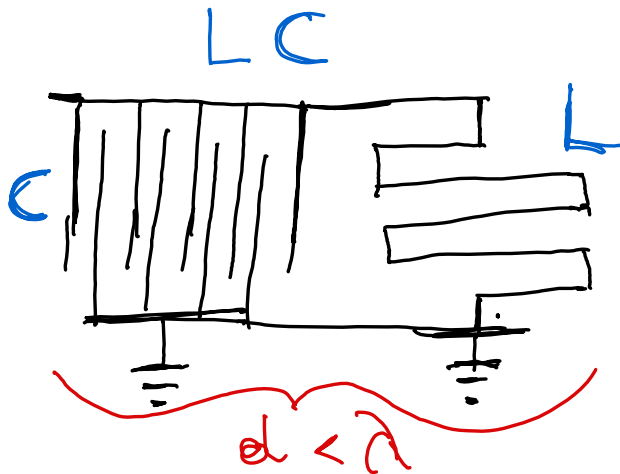(2)

There are two types of on-chip electronic components:  
lumped elements and distributed elements.


The two types are distinguished by how large they are by comparison with the wavelength of microwave radiation at the relevant frequency: For lumped elements, the size " $d$ " of the components is much smaller than the wavelength,  $d \ll \lambda$ ; whereas for distributed elements, the size of the component is roughly the same size as  $\lambda$  or bigger:  $d \gtrsim \lambda$ . For GHz photons  $\Rightarrow \lambda \sim \text{cm}$



The low frequency dynamics of this system are fully captured by two effective parameters  $L, C$ .

The finite dimension of the system "el" can be neglected.

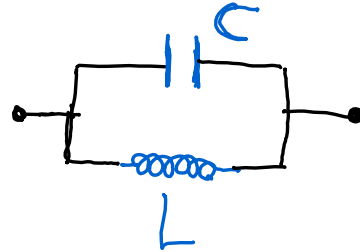The system is represented by a LUMPED ELEMENT model




# Quantization of the LC resonator

Consider

Electric field :  $Q^2/2C$

Magnetic :  $\Phi^2/2L$

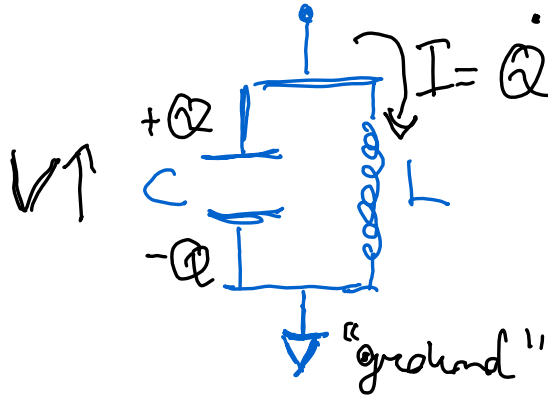


Faraday's law of induction  $\dot{\Phi} = V$

$$\Rightarrow \ddot{\Phi} = \dot{V} = \frac{\dot{Q}}{C} = -\frac{I}{C} = -\frac{\dot{\Phi}}{LC} = -\omega_0^2 \Phi, \quad \omega_0 = \sqrt{\frac{1}{LC}}$$

# Electronic Harmonic Oscillator

(6)

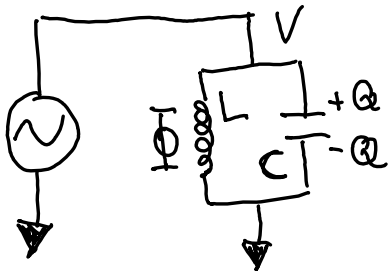

- charge on capacitor

$$Q = CV$$

- flux in the inductor

$$\Phi = LI$$

- voltage across oscillator

$$V = \frac{Q}{C} = -L \dot{I} = -\dot{\Phi}$$

Hamiltonian

$$H = \frac{CV^2}{2} + \frac{LI^2}{2} = \frac{Q^2}{2C} + \frac{\Phi^2}{2L}$$


electrostatic  
energy

magnetic  
energy

- Compare to mechanical harmonic oscillator

$$H = \frac{p^2}{2m} + \frac{kx^2}{2}$$

kinetic K + potential U

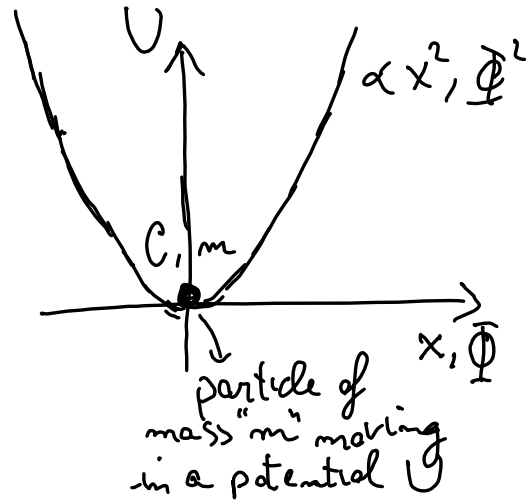

# Characteristic quantities

## mechanical

position  $x$

momentum  $p$

mass  $m$

spring constant  $K$

resonance freq.  $\omega = \sqrt{\frac{K}{m}}$

## electronic

flux  $\Phi$

charge  $Q$

capacitance  $C$

inverse inductance  $\frac{1}{L}$

$\omega = \sqrt{\frac{1}{LC}}$

- quantum mechanical operators

$$\hat{x} = x$$

$$\hat{p} = -i\hbar \frac{\partial}{\partial x}$$

$$\hat{\Phi} = \Phi$$

$$\hat{Q} = -i\hbar \frac{\partial}{\partial \Phi}$$

- commutation relation

$$[\hat{x}, \hat{p}] = i\hbar$$

$$[\hat{\Phi}, \hat{Q}] = i\hbar \Leftrightarrow$$

$$\left[ 2\pi \frac{\hat{\Phi}}{\Phi_0}, \frac{Q}{2e} \right] = [\hat{F}, \hat{N}] = i$$

## Harmonic oscillator

conjugate variables

$$\frac{\partial H}{\partial \Phi} = \frac{\Phi}{L} = I = \dot{Q}$$

$$\frac{\partial H}{\partial Q} = \frac{Q}{C} = V = -L\dot{I} = -\dot{\Phi}$$

$$\left[ \begin{array}{l} x, p \text{ are canonical} \\ \Phi, Q \text{ variables} \end{array} \right]$$

# Hamiltonian operator

(8)

- using conjugate variables  $Q, \Phi$

$$\hat{H} = \frac{\hat{Q}^2}{2C} + \frac{\hat{\Phi}^2}{2L} = -\frac{\hbar^2}{2C} \frac{\partial^2}{\partial \Phi^2} + \frac{1}{2L} \Phi^2$$

- using creation and annihilation operators

$$\hat{a}^+ = \frac{1}{\sqrt{2\hbar Z_c}} \left( Z_c \hat{Q}^+ - i \hat{\Phi}^+ \right) \text{ creation operators}$$

$$\hat{a} = \frac{1}{\sqrt{2\hbar Z_c}} \left( Z_c \hat{Q} + i \hat{\Phi} \right) \text{ annihilation}$$

with  $Z_c = \sqrt{L/C}$  impedance of oscillator

$$\hat{H} = \hbar \omega \left( \hat{a}^+ \hat{a} + \frac{1}{2} \right)$$

$\hat{a}^+ \hat{a} = n$  number operators




• Properties of  $\hat{a}^+$  and  $\hat{a}$

$$\hat{a}^+ |n\rangle = \sqrt{n+1} |n+1\rangle$$

$$\hat{a} |n\rangle = \sqrt{n} |n-1\rangle$$

$$\hat{a}^+ \hat{a} |n\rangle = n |n\rangle$$

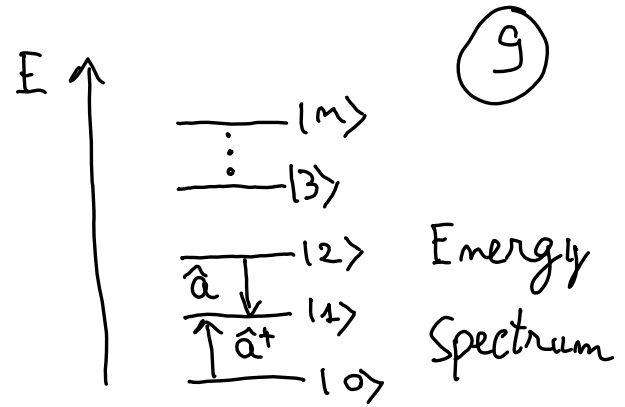

with  $|n\rangle$  number (Fock) state  
of harmonic oscillator

• relation to  $\hat{Q}$  and  $\hat{\Phi}$

$$\hat{Q} = \sqrt{\frac{\hbar}{2Z_c}} (\hat{a}^+ + \hat{a}) \rightarrow \text{related to electric field stored on capacitor}$$


$$\hat{\Phi} = i\sqrt{\frac{\hbar Z_c}{2}} (\hat{a}^+ - \hat{a}) \rightarrow \text{related to magnetic field stored in inductor}$$

or  $\hat{V} = \sqrt{\frac{\hbar \omega}{2C}} (\hat{a}^+ + \hat{a})$  with  $\omega = \frac{1}{\sqrt{LC}}$  and  $V = \frac{Q}{C}$  and  $I = \frac{\Phi}{L}$

$$\hat{I} = i\sqrt{\frac{\hbar \omega}{2L}} (\hat{a}^+ - \hat{a})$$

# Dissipation in the Harmonic Oscillator

(10)

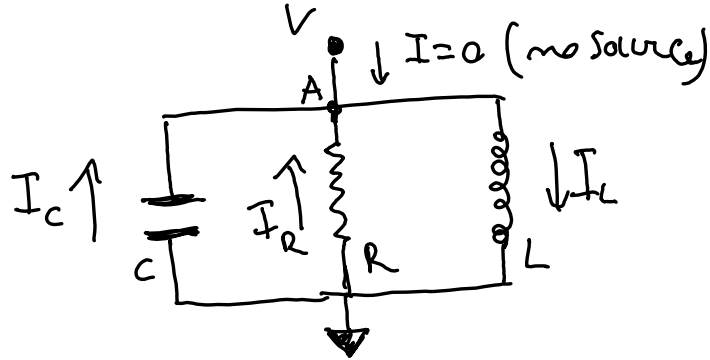

with

- current through resistor

$$I_R = V/R$$

- displacement current

$$I_C = \dot{Q}_C = C \dot{V}$$

- voltage across inductor

$$V = -L \dot{I}_L$$

- Kirchoff law at point A

$$I_L = I_R + I_C + I$$

$$I_L - C \dot{V} - \frac{V}{R} = 0 \quad (\text{same voltage at A})$$

$$I_L - C(-L \ddot{I}_L) + \frac{L}{R} \dot{I}_L = \frac{1}{LC} I_L + \ddot{I}_L + \frac{1}{RC} \dot{I}_L = 0$$

differential equation for current through inductor

Solution  $I_L(t) = I_L(0) e^{\lambda t}$  with  $\lambda_{1,2} = \frac{1}{2LC} \left( -\frac{L}{R} \pm \sqrt{\left(\frac{L}{R}\right)^2 - 4LC} \right)$

# Energy Decay Rate

(11)

- underdamped oscillator ( $4LC \gg L/R$ )

$$\lambda_{1,2} = -\frac{1}{2RC} \pm i \frac{1}{\sqrt{LC}} = -2 \pm i\omega$$

with  $2 = \frac{1}{2RC} = \frac{1}{\tau}$  amplitude decay constant

$\tau = 2RC$  " " time


$\omega = 1/\sqrt{LC}$  oscillator frequency

- energy decay rate

$$\bar{E} \propto \frac{1}{2} L I_L^2 \propto e^{-\frac{1}{RC} t}$$

with  $k = \frac{1}{RC}$  energy decay rate



$T_k = RC$  " " time

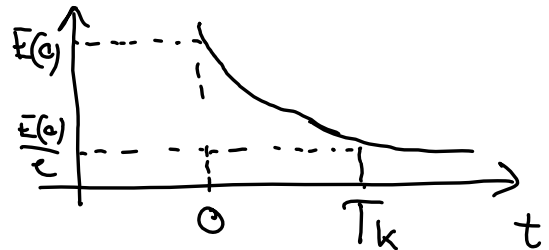

# Spectral Response of Damped Harmonic Oscillator

- driven damped oscillator

(12)

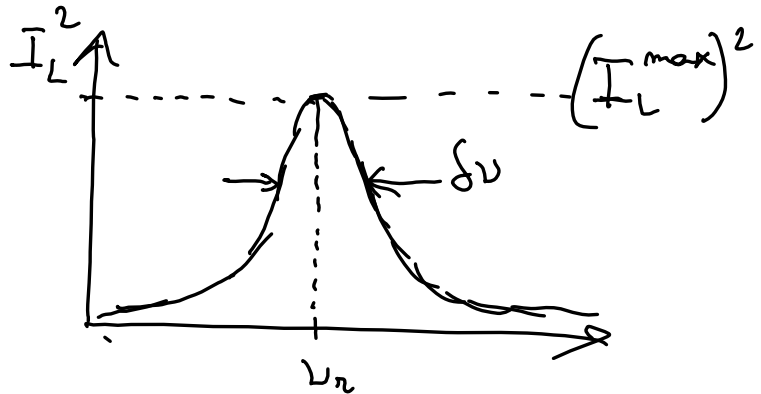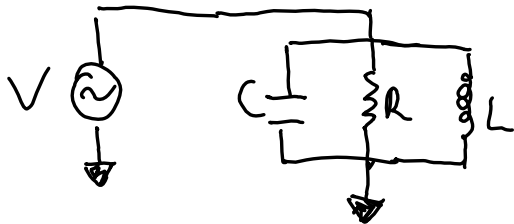


Lorentzian line shape

$$I_L^2(\nu) = (I_L^{\max})^2 = \frac{\delta\nu / \pi}{(\nu - \nu_r)^2 + \delta\nu^2}$$

with  $\delta\nu$ : full width of line at half max

# Internal and External Dissipation

13

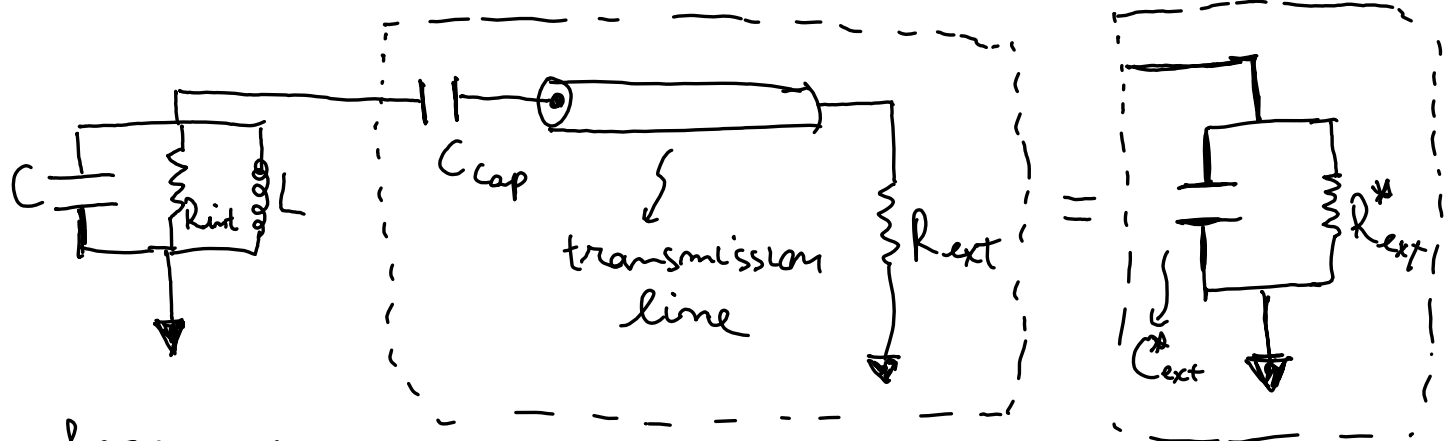

harmonic  
oscillator

external  
circuitry

- total effective resistance  $\frac{1}{R_{tot}} = \frac{1}{R_{int}} + \frac{1}{R_{ext}^*}$
- total effective capacitance

$$C_{tot} = C_{int} + C_{ext}^*$$

- energy decay time of combined system  $T_k = R_{tot} C_{tot}$


external  
contribution  
to energy  
decay

frequency  
shift  
due to external  
circuit


# Transmission line resonator

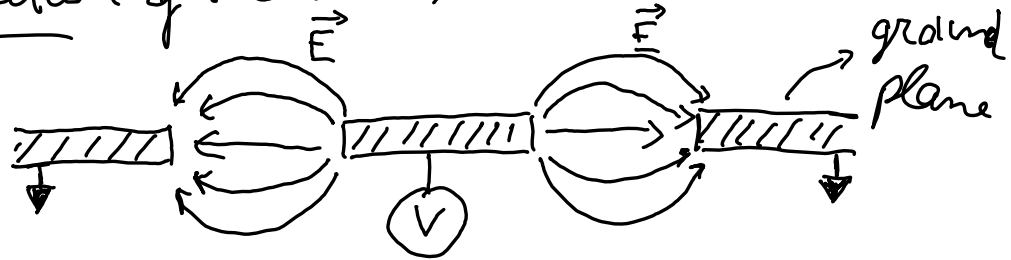(14)

Field distribution of the transmission line




Wave propagation in a transmission line

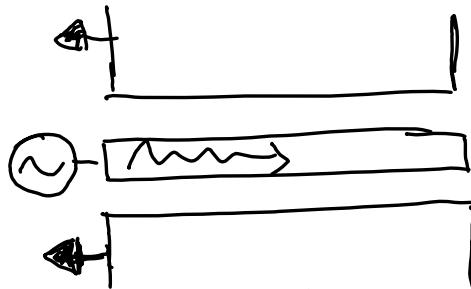

$$E = E_0 e^{i(kx - \omega t)}$$

$$\omega = c_{\text{eff}} k = \frac{c}{\sqrt{\epsilon}} \frac{2\pi}{\lambda}$$

Electric field at the boundary

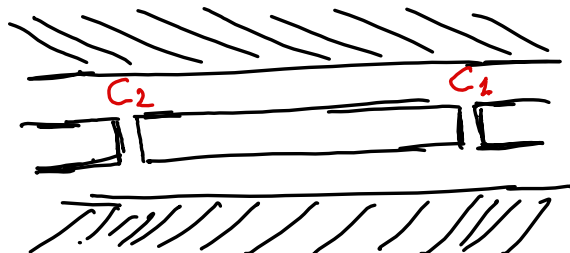

Capacitors ( $C_i$ ) as mirrors:  
defining modes for the  
current, so antinodes  
(maximum) for the voltage.

Fundamental mode  $\lambda/2$  mode

15




Higher harmonics:  $2\frac{\lambda}{2}$ ;  $3\frac{\lambda}{2}$ ;  $4\frac{\lambda}{2}$ ; ...;  $n\frac{\lambda}{2}$

Resonance frequency?

$$\left. \begin{aligned} \omega &= c_{\text{eff}} \frac{2\pi}{\lambda} \\ l &= \frac{\lambda}{2} n \end{aligned} \right\} \omega = c_{\text{eff}} \frac{2\pi}{2l} = \frac{\pi c_{\text{eff}}}{l} n$$

Excitation spectrum:

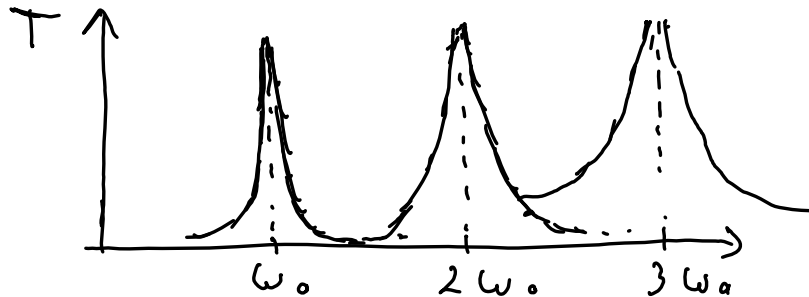

"Harmonic oscillator"

# General procedure to find Hamiltonian

(16)

① Set up Lagrange function

$$\mathcal{L} = T - V = \underbrace{\frac{1}{2} C \dot{\Phi}^2}_{\text{"kinetic"}} - \underbrace{\frac{1}{2L} \Phi^2}_{\text{"potential"}}$$

② Legendre transformation

conjugate variable  $Q = \frac{\partial \mathcal{L}}{\partial \dot{\Phi}} = C \dot{\Phi}$

③ Hamiltonian function

$$H = \dot{\Phi} Q - \mathcal{L} = \frac{Q^2}{C} - \frac{Q^2}{2C} - \left( -\frac{\Phi^2}{2L} \right) = \frac{Q^2}{2C} + \frac{\Phi^2}{2L}$$

④ Quantize  $Q \rightarrow \hat{Q}$  ;  $\Phi \rightarrow \hat{\Phi}$  with  $[\hat{\Phi}, \hat{Q}] = i\hbar$

⑤ Express  $\hat{H}$  in terms of annihilation and creation operators,  
 $\hat{\Phi} = \left[ \frac{\hbar \omega_0 L}{2} \right]^{\frac{1}{2}} (a + a^\dagger)$  ;  $\hat{Q} = \left[ \frac{\hbar \omega_0 C}{2} \right]^{\frac{1}{2}} i (a - a^\dagger)$



to obtain  $\hat{H} = \hbar \omega_0 a^\dagger a + \text{const} ; [a, a^\dagger] = 1$

(17)

Thus procedure is generally applicable to more complicated circuits.

• Properties of Quantum Harmonic Oscillator:

The ground state satisfies  $a|0\rangle = 0$

Eigenstates of  $a^\dagger a = \hat{n}$  are called "Fock states"

$$a^\dagger a |n\rangle = n |n\rangle, \quad n \in \{0, 1, 2, \dots\}$$

The number  $n$  corresponds to the number of elementary excitations, i.e. photons at frequency  $\omega_0$ .

Applying  $a$  ( $a^\dagger$ ) to state  $|n\rangle$  raises (lowers)  $n$  by 1:

$$a^\dagger |n\rangle = \sqrt{n+1} |n+1\rangle ; \quad a |n\rangle = \sqrt{n} |n-1\rangle$$

which follows from the commutation relation.

$$a^\dagger a (a^\dagger |n\rangle) = a^\dagger (1 + a^\dagger a) |n\rangle = (n+1) a^\dagger |n\rangle \sim |n+1\rangle \quad (18)$$

The zero-point fluctuations (zpf) of  $\hat{\Phi}$  and  $\hat{Q}$  of the ground state are

$$\langle 0 | \hat{\Phi}^2 | 0 \rangle = \Phi_{zpf}^2 \quad ; \quad \langle 0 | \hat{Q}^2 | 0 \rangle = Q_{zpf}^2$$

- An important class of states are "coherent states" defined:  
 $a |\alpha\rangle = \alpha |\alpha\rangle, \quad \alpha \in \mathbb{C}$


They are important because they have dynamics closely resembling the behaviour of a classical harmonic oscillator.

$$e^{-i\hat{H}_z t} |\alpha_0\rangle = |\alpha(t)\rangle = |\alpha_0 e^{-i\omega t}\rangle$$

$$\langle \alpha(t) | \hat{\Phi} | \alpha(t) \rangle = 2 \Phi_{zpf} \alpha_0 \cos(\omega t)$$

$$\langle \alpha(t) | \hat{Q} | \alpha(t) \rangle = 2 Q_{zpf} \alpha_0 \sin(\omega t)$$

$$|\alpha\rangle = e^{-\frac{1}{2}|\alpha|^2} \sum_{n=0}^{\infty} \frac{\alpha^n}{\sqrt{n!}} |n\rangle \quad (\text{in the Fock state representation})$$

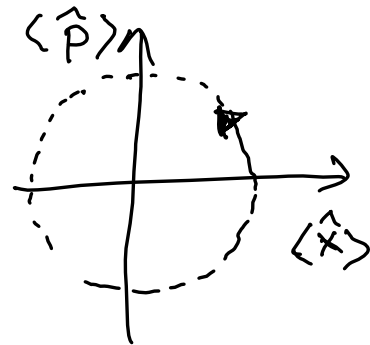


# Quantization of coupled resonator systems

(19)

Consider the electric circuit

with Lagrange function

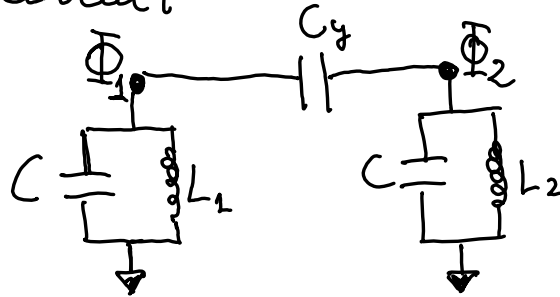

$$\mathcal{L} = \frac{1}{2} C \dot{\Phi}_1^2 + \frac{1}{2} C \dot{\Phi}_2^2 + \frac{1}{2} C_y (\dot{\Phi}_2 - \dot{\Phi}_1)^2 - \frac{\Phi_1^2}{2L_1} - \frac{\Phi_2^2}{2L_2}$$



Applying the canonical transformation ....

$$H = \hbar \omega_1 a^\dagger a + \hbar \omega_2 b^\dagger b + \hbar y (a - a^\dagger)(b - b^\dagger)$$

[see exercise]
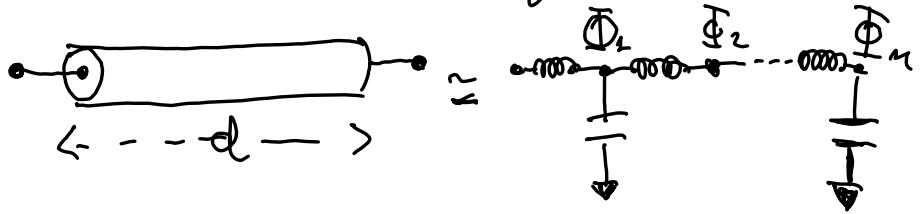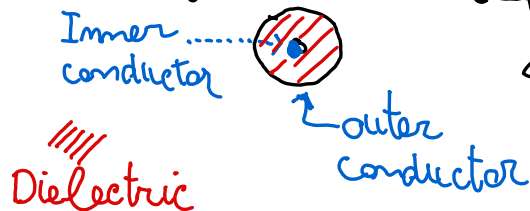
# Transmission line (distributed) resonators (20)

A finite length transmission line, e.g. a coaxial waveguide



Can be represented by a series of inductances and capacitors (to ground).

In the continuum limit  $n \rightarrow \infty$  the flux variables  $\Phi_i$  become a position-dependent field  $\Phi(x)$  and the Lagrange function is

$$\mathcal{L} = \int_0^d dx \left\{ \frac{C}{2} \dot{\Phi}(x)^2 - \frac{1}{2l} (2x \Phi(x))^2 \right\} \quad \left\{ \begin{array}{l} \text{with } C \text{ and } l \text{ are} \\ \text{capacitance and} \\ \text{inductance per} \\ \text{unit length} \end{array} \right.$$

Taking the boundary condition of vanishing (21) current at the two open ends, we can express  $\Phi(x)$  in terms of the normal modes

$$\Phi(x) = \sum_{n=1}^{\infty} \phi_n \cos(k_n x), \quad k_n = n \frac{\pi}{d}$$

resulting in

$$\mathcal{L} = \frac{1}{2} \sum_n \left( C \dot{\phi}_n^2 - \frac{1}{L_n} \phi_n^2 \right) \quad \text{with}$$

$$C = \frac{c d}{2}$$

$$L_n = \frac{2 \hbar d}{\pi^2 n^2}$$

Introducing  $q_n = \frac{2 \mathcal{L}}{2 \dot{\phi}_n^2}$  we obtain

$$H = \frac{1}{2} \sum_{n=1}^{\infty} \left( \frac{q_n^2}{C} + \frac{\phi_n^2}{L_n} \right) = \text{sum of harmonic oscillators}$$

$$= \sum_{n=1}^{\infty} \omega_n a_n^+ a_n$$

$$\text{with } \omega_n = \frac{1}{\sqrt{L_n C}} = n \frac{\pi v}{d}$$

$$\text{and } v = \frac{1}{\sqrt{\hbar c}} \quad \text{"phase velocity"}$$