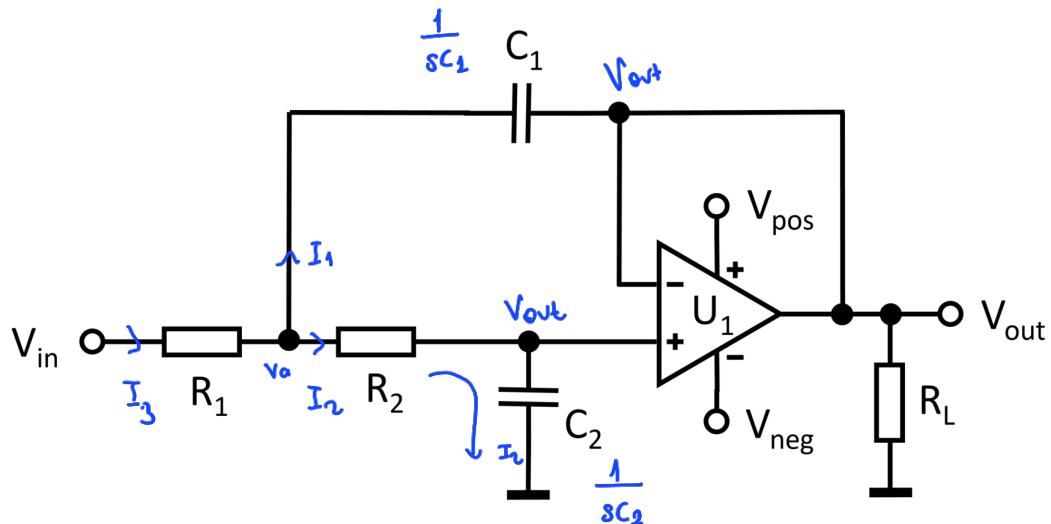



# Exercise set #5

## Exercise 1:

We want to analyze the following circuit using *Ltspice*:



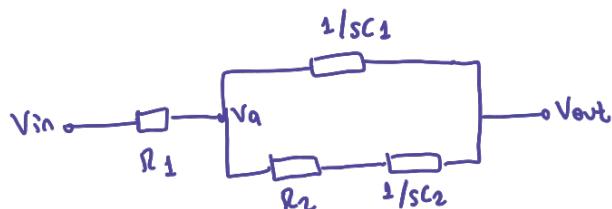- a) Draw the circuit and use the following values for the components:



1

$$\frac{V_{in} - V_a}{R_2} = \frac{V_a - V_{out}}{\frac{1}{2\pi C_1}} + \frac{V_a - V_{out}}{R_2 + \frac{1}{2\pi C_2}}$$

$R_1$	$15 k\Omega$	✓
$R_2$	$15 k\Omega$	✓
$R_L$	$50 \Omega$	✓
$C_1$	$225 pF$	✓
$C_2$	$115 pF$	✓
$U1$	<i>UniversalOpamp2</i>	✓
$V_{pos}$	$5 V$	✓
$V_{neg}$	$-5 V$	✓

✓ b) Simulate the circuit and plot  $V_{out}$  as a function of time, when  $V_{in}$  is a sinusoidal signal with an amplitude of  $1 V$ , a DC offset of  $0 V$  and frequency  $f = 10 kHz$ .  $\rightarrow T = \frac{1}{10^4} = \frac{1}{10^6} = 10^{-4} sec = 10^7 \times 10^{-3} = 0.1 msec$

✓ c) Repeat the simulation for  $f = 5 kHz$ ,  $f = 50 kHz$ ,  $f = 100 kHz$  and  $f = 500 kHz$ . What does the circuit do?

✓ d) Find  $f_C$  for which the amplitude of  $V_{out}$  is  $3 dB$  lower than  $V_{in}$ .

✓ e) Repeat d) for  $C_2 = 65 pF$ ,  $C_2 = 200 pF$  and  $C_2 = 250 pF$ .

✓ f) Find a value for  $C_2$  such that  $f_C = 30 kHz$ .

✓ g) Simulate the circuit and plot  $V_{out}$  as a function of time, when  $V_{in}$  is a rectangular signal with an amplitude of  $1 V$ , a DC offset of  $0 V$  and frequency  $f = 20 kHz$ . What do you observe?


$$\frac{1}{20^4} = \frac{1}{10} \times \cancel{\frac{10^3}{nsec}} = 0.05 msec = 50 nsec$$

h) Plot the spectrum of  $\underline{\underline{V_{out}}}$ .


i) Measure the average power required at  $V_{pos}$ .

j) What will happen to  $V_{out}$  if  $V_{in}$  is a sum of two sinusoidal signals with amplitudes of  $1 V$ , DC offsets of  $0 V$  and frequencies  $f_1 = 10 kHz$  and  $f_2 = 100 kHz$ ? What about  $f_1 = 10 kHz$  and  $f_2 = 40 kHz$ ?


a)

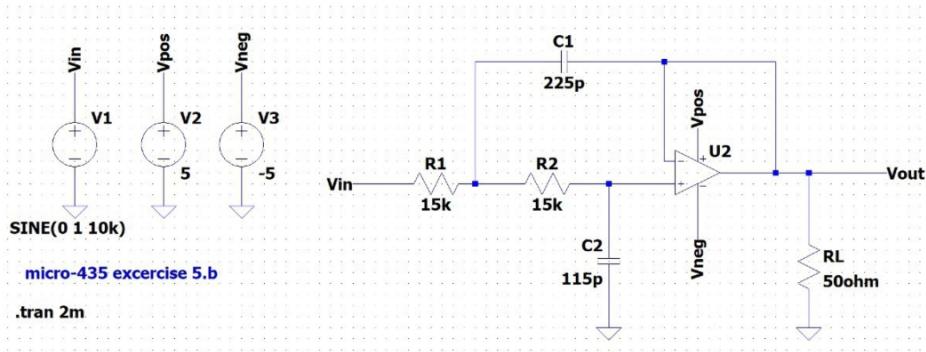


b)


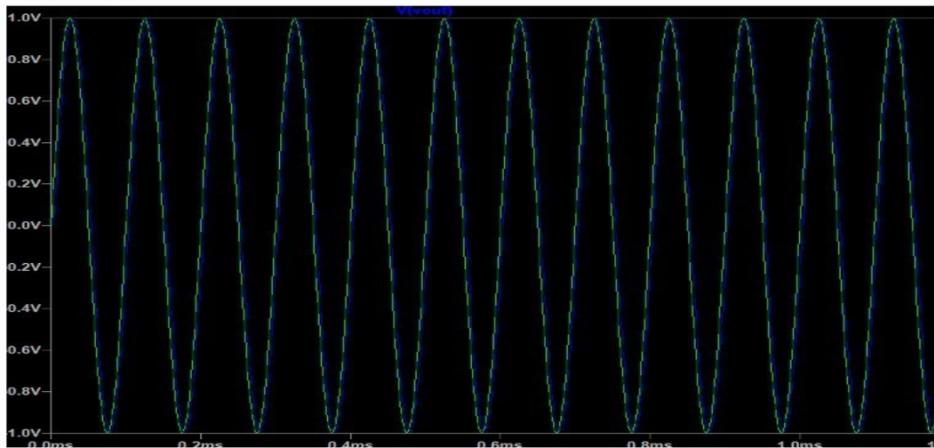


c)

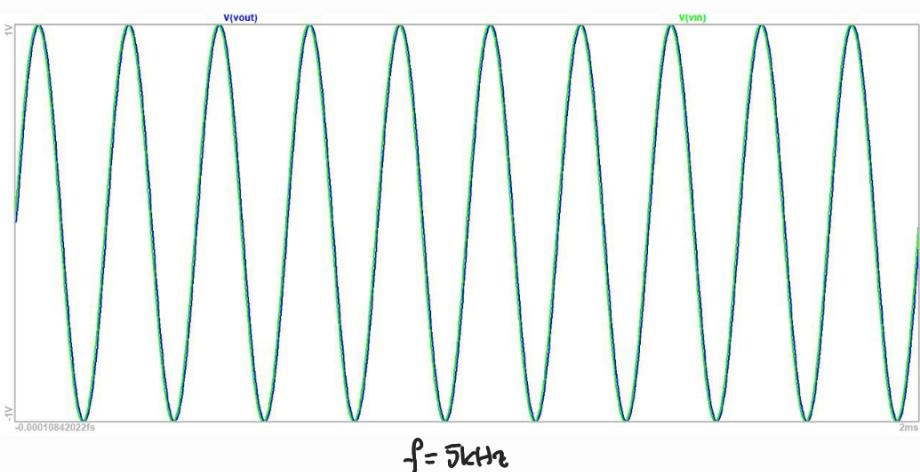



$$f = 5\text{kHz}$$

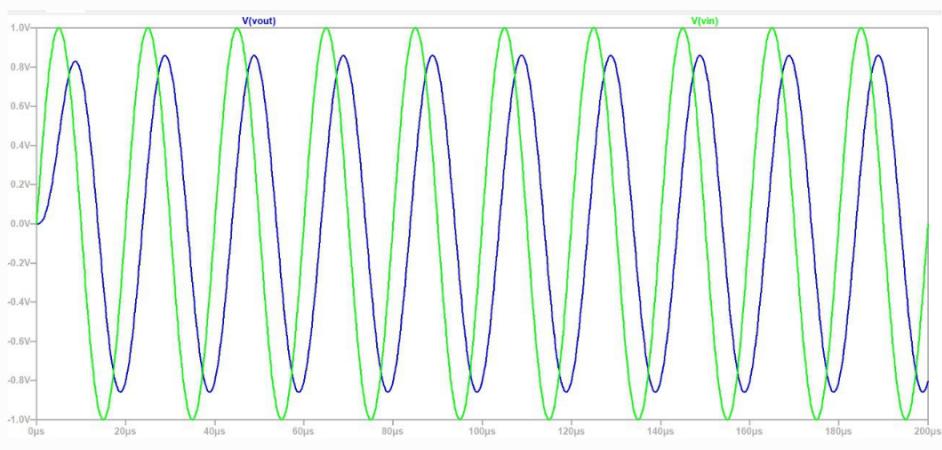

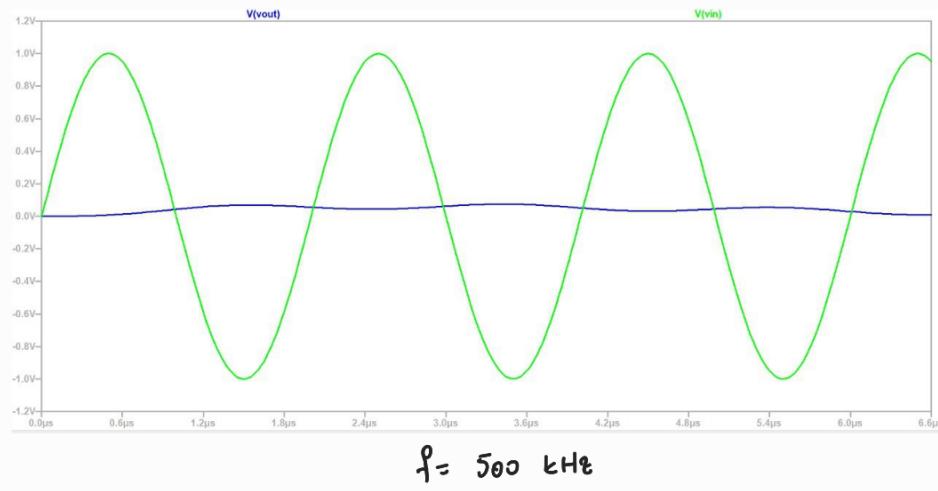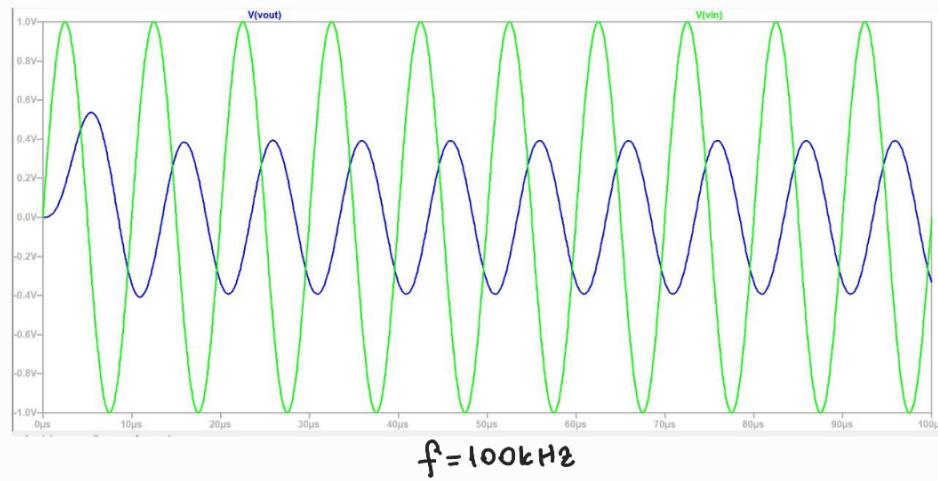


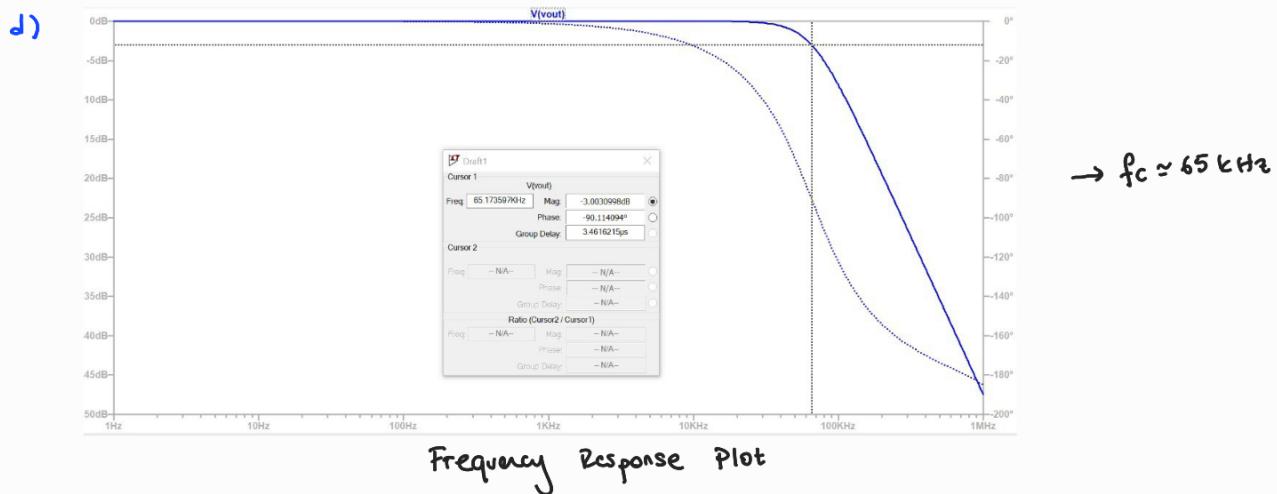Increasing frequency yields decrease in voltage.



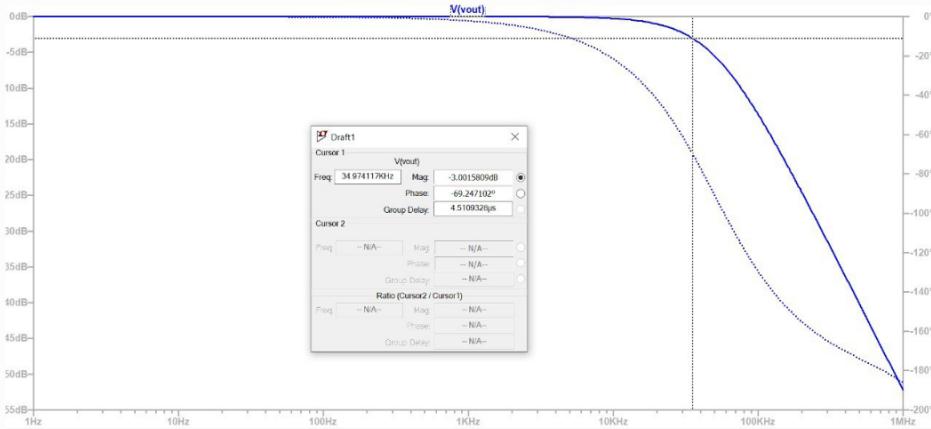


Bode Plot when  $C_2 = 200\text{pF}$

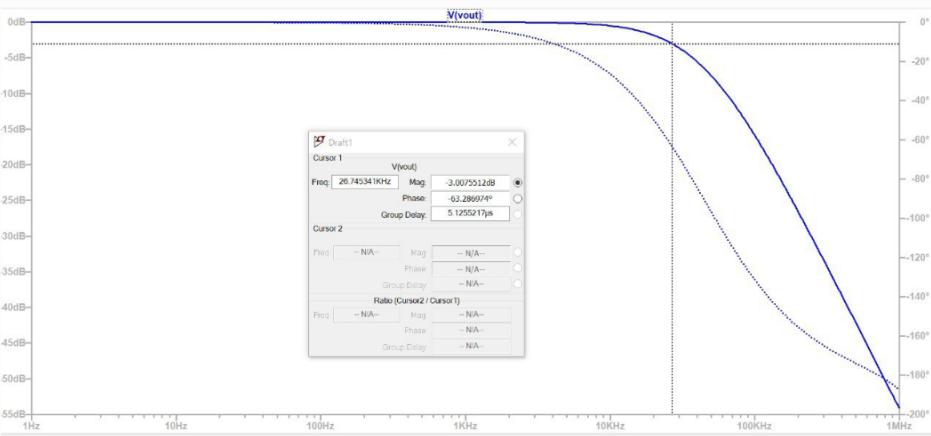

$f_c \approx 27\text{ kHz}$

Bode Plot when  $C_2 = 250\text{pF}$

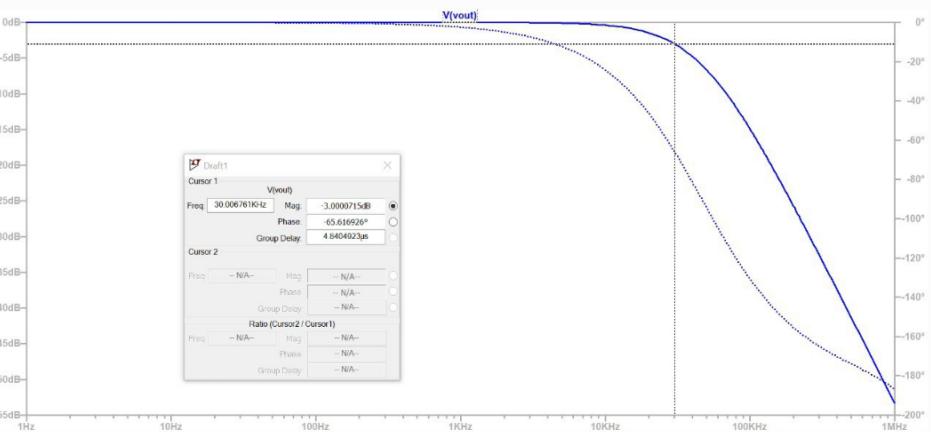f) From my intuition if  $C_2 = 200\text{pF} \rightarrow f_c = 35\text{kHz}$  &  $C_2 = 250\text{pF} \rightarrow f_c = 27\text{kHz}$ ,  $C \approx 227\text{pF} \rightarrow f_c = 30\text{kHz}$



g)

